

GUJARAT TECHNOLOGICAL UNIVERSITY
BE –SEMESTER 1&2(NEW SYLLABUS)EXAMINATION- WINTER 2018

Subject Code: 3110016**Date: 08-01-2019****Subject Name: basic electronics****Time: 10:30 am to 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		Marks
Q.1	(a) Explain V-I characteristic of tunnel diode.	03
	(b) What is zener breakdown? What is avalanche breakdown? Compare both the type of breakdown.	04
	(c) Write a short note: V-I characteristic of P-N junction diode.	07
Q.2	(a) Design and explain basic NAND gate using DTL logic.	03
	(b) Explain following gate using their truth table, logic symbol and equation. Ex-NOR, NAND, NO	04
	(c) Draw and Explain bridge rectifier. Explain advantage and disadvantage of bridge rectifier over full wave rectifier.	07
	OR	
	(c) Write a short note: Biased clipper circuit.	07
Q.3	(a) Derive the relation between current gain α and β	03
	(b) What is DC load line? Explain with necessary diagram.	04
	(c) Draw and explain input and output characteristic of transistor in common emitter configuration.	07
	OR	
Q.3	(a) What is stability factor? Explain.	03
	(b) Give comparison between CE, CB and CC configuration of transistor.	04
	(c) What are the different method for biasing the transistor. Explain any two method with necessary circuit diagram.	07
Q.4	(a) Why biasing circuits are required?	03
	(b) Explain why NAND and NOR gate are called universal gate?	04
	(c) Explain application of transistor as a switch.	07
	OR	
Q.4	(a) List out the salient feature of emitter follower.	03
	(b) Explain various properties of CB amplifier.	04
	(c) Draw and explain the transistor a.c. equivalent circuit.	07
Q.5	(a) Give comparison of BJT and JFET.	03
	(b) Draw and explain the self bias circuit of FET.	04
	(c) Draw and explain various characteristic of JFET	07
	OR	
Q.5	(a) What are the advantage of N-Channel MOSFET over P-Channel MOSFET.	03
	(b) Explain the application of FET as a buffer amplifier.	04
	(c) Write a short note: E-Type MOSFET	07

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-I &II (NEW) EXAMINATION – SUMMER-2019****Subject Code: 3110016****Date: 07/06/2019****Subject Name: Basic Electronics****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

Marks

Q.1	(a)	Differentiate between insulator, conductor and semiconductor	03
	(b)	Explain forward bias PN junction diode with diagram	04
	(c)	Explain full wave bridge rectifier with neat diagram	07
Q.2	(a)	Explain LED diode	03
	(b)	State different types of diodes. Describe process of testing diode with multi meter.	04
	(c)	What is break down diode?? Explain working of zener break down and avalanche break down	07
OR			
	(c)	Why biasing is important in transistor? Explain voltage divider bias with diagram.	07
Q.3	(a)	What is use of coupling and bypass capacitor?	03
	(b)	Explain PIN photo diode	04
	(c)	Draw the circuit of transistor in CE configuration. Sketch the output characteristics and explain active, saturation and cutoff regions	07
OR			
Q.3	(a)	What is varactor diode? How capacitance of a diode varies with reverse voltage?	03
	(b)	Explain AC loadline with respect to BJT	04
	(c)	Compare CE, CB and CC configuration with respect to different transistor characteristics	07
Q.4	(a)	What is FET? State important features of FET.	03
	(b)	Compare BJT and FET	04
	(c)	Write short note on MOSFET.	07
OR			
Q.4	(a)	Explain clipping circuit	03
	(b)	Explain (i) Unipolar device (ii) Transconductance	04
	(c)	Write shortnote on JFET	07
Q.5	(a)	Draw the symbol of NPN and PNP transistor. What is use of transistor?	03
	(b)	Among TTL and CMOS digital logic family which one is better and why?	04
	(c)	Draw symbol and explain truth table of all basic logic gates	07
OR			
Q.5	(a)	State advantage of transistor	03
	(b)	Explain (i)universal gate (ii) EX-OR logic gate	04
	(c)	Give comparison between different types of digital logic families	07

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER- I & II (NEW) EXAMINATION – WINTER 2019****Subject Code: 3110016****Date: 06/01/2020****Subject Name: Basic Electronics****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		Marks
Q.1	(a) Draw the circuit diagram of Half wave rectifier.	03
	(b) Explain the bridge rectifier with diagrams.	04
	(c) Determine the V_o for the network shown in figure 1	07

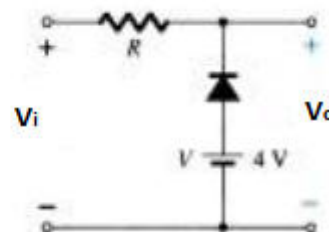
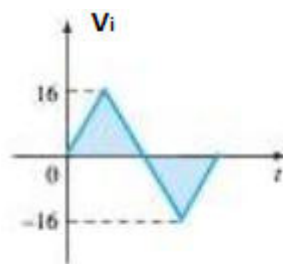


Figure 1

Q.2	(a) Explain Varactor diode and varistor.	03
	(b) Why Zener diode can be used as voltage regulator? Explain Zener as voltage regulator with necessary diagram	04
	(c) Compare the logic families and explain any one of them.	07
OR		
	(c) Explain Ex-OR and Ex- NOR gate with truth table and construct OR gate using diodes.	07
Q.3	(a) Explain about DC load line and Bias point of transistor	03
	(b) Explain the working of PIN Diode.	04
	(c) Briefly explain the h-parameters and draw h-parameter based equivalent circuit for CE transistor and derive equation for input impedance, output impedance and voltage gain.	07
OR		
Q.3	(a) Write truth table of AND, NAND and NOR gates.	03
	(b) Explain the selection of a Q point for a transistor bias circuit and discuss the limitations on the output voltage swing.	04
	(c) Explain the difference between clipping and clamping circuit. A positive voltage clamping circuit and a positive voltage clipping circuit each have ± 12 V square Wave input. Sketch the output waveform for each circuit.	07
Q.4	(a) Draw voltage multiplier circuit.	03
	(b) Explain Transconductance and switching in FET.	04

- (c) Explain the Depletion region and drain characteristics of n channel JFET. **07**

OR

- Q.4** (a) Discuss about VI characteristic of Ideal Diode. **03**
 (b) Explain FET as an Amplifier. **04**
 (c) Determine the voltage V_o for the network of Figure 2. **07**
 Give explanation for your answer.

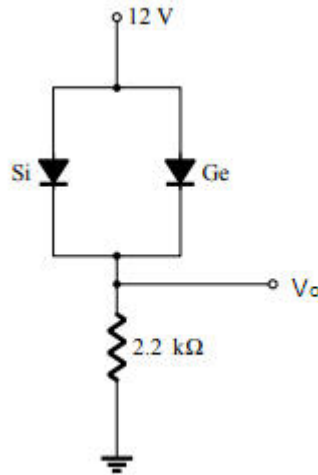


Figure 2

- Q.5** (a) Explain the working of Transistor as Switch **03**
 (b) Write a short note on E MOSFET as an Amplifier. **04**
 (c) Design a series noise clipping circuit which rectify the noise signal with amplitude lower than $\pm V_F$. **07**

OR

- Q.5** (a) Explain the AC load line of transistor. **03**
 (b) Draw and explain seven segment display. **04**
 (c) Compare BJT with FET and explain D MOSFET. **07**

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- SEMESTER-I & II(NEW)EXAMINATION – SUMMER 2022****Subject Code:3110016****Date:24-08-2022****Subject Name:Basic Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) What is a diode? Write its types and applications.	03
	(b) Explain the diode V-I characteristics of ideal and practical PN junction semiconductor diode.	04
	(c) Enumerate the different types of clipping circuits with their different names and input-output waveforms.	07
Q.2	(a) Why are junction transistors called bipolar devices?	03
	(b) The metal lead of the p-side of a p-n diode is soldered to the metal lead of the p-side of another p-n junction diode. Will the structure form an n-p-n transistor? If not, why?	04
	(c) Sketch the circuit of the common collector mode of BJT and its output characteristics. Derive the expression for the collector current and gain.	07
	OR	
	(c) Draw the fixed-biased circuit by considering an n-p-n transistor in the CE mode. Derive the expressions for stability factors. What are the functions of the coupling capacitors?	07
Q.3	(a) Write a short note on the optocoupler device?	03
	(b) Explain the sixteen segment display and its applications with the necessary circuit diagram.	04
	(c) Draw the approximate hybrid model for any transistor configuration at low frequencies. Show that only h_{ie} and h_{fe} are essential in the model. Is the approximation justified?	07
	OR	
Q.3	(a) Explain the varactor diode.	03
	(b) Explain the construction of the solar cell with its operational principle.	04
	(c) What is self-bias? Draw the circuit showing self-bias of an n-p-n transistor in the CE mode. Explain physically how the self-bias improves stability.	07
Q.4	(a) What is MOSFET device? Draw its construction diagram.	03
	(b) Write short notes on the following : (i) Advantages of JFET (ii) Difference between MOSFET and JFET	04
	(c) Compare the different characteristics of the following semiconductor devices: bipolar junction transistor, field-effect transistor.	07
	OR	
Q.4	(a) How will you determine the drain characteristics of JFET? What do they indicate?	03
	(b) Explain the common drain configuration for a JFET.	04
	(c) Explain the JFET parameters and establish the relationship between them	07

- Q.5** (a) What is the thermal runaway in transistors, and how can it be avoided? **03**
(b) What is an Early effect, and how can it account for the CB input characteristics?. **04**
(c) What do you mean by the logic gate and its types? Explain the universal logic gates. **07**

OR

- Q.5** (a) What is the ac load line in the transistor? Write its significance. **03**
(b) The value of alpha increases with the increasing reverse-bias voltage of the collector junction. Why? **04**
(c) Explain the logic families and their types. Describe the characteristics of the same. **07**

GUJARAT TECHNOLOGICAL UNIVERSITY
BE - SEMESTER-I & II(NEW) EXAMINATION – WINTER 2022

Subject Code:3110016**Date:16-03-2023****Subject Name:Basic Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	Marks
Q.1 (a) Define between insulator, conductor and semiconductor.	03
(b) What is Zener breakdown? What is avalanche breakdown? Compare both the type of breakdown.	04
(c) Explain full wave bridge rectifier with neat diagram.	07
Q.2 (a) Design and explain basic NAND gate using DTL logic.	03
(b) Discuss different types of diodes. Describe process of testing diode with multi meter.	04
(c) Write a short note: V-I characteristic of P-N junction diode.	07
OR	
(c) Why biasing is important in transistor? Explain voltage divider bias with diagram.	07
Q.3 (a) Explain about DC load line of transistor.	03
(b) Explain PIN photo diode.	04
(c) Draw and explain input and output characteristic of transistor in common emitter configuration.	07
OR	
Q.3 (a) What is varactor diode? How capacitance of a diode varies with reverse voltage?	03
(b) Explain the selection of a Q point for a transistor bias circuit and discuss the limitations on the output voltage swing.	04
(c) Compare CB and CC configuration with respect to different transistor characteristics.	07
Q.4 (a) Draw voltage multiplier circuit.	03
(b) Explain (i) Unipolar device (ii) Transconductance.	04
(c) Explain application of transistor as a switch.	07
OR	
Q.4 (a) Explain FET as an Amplifier.	03
(b) Explain why NAND and NOR gate are called universal gate?	04
(c) Explain the Depletion region and drain characteristics of n channel JFET.	07
Q.5 (a) Among TTL and CMOS digital logic family which one is better and why?	03
(b) Draw and explain the self-bias circuit of FET.	04
(c) Write a short note: E-Type MOSFET.	07
OR	
Q.5 (a) Derive the relation between current gain α and β .	03
(b) What are the advantages of N-Channel MOSFET over P-Channel	04

MOSFET?

- (c) Draw symbol and explain truth table of all basic logic gates.

07

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- SEMESTER-I & II(NEW) EXAMINATION – SUMMER 2023****Subject Code:3110016****Date:11-08-2023****Subject Name:Basic Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Explain zener diode as a Voltage regulator.	03
	(b) Compare Half wave rectifier and Full wave bridge rectifier for following parameters.	04
	(i) Average DC Voltage	
	(ii) Ripple Factor	
	(iii) PIV	
	(iv) Rectifier Efficiency	
	(c) Illustrate the need of clipper circuit and explain Positive clipper and negative clipper with necessary diagram and waveforms.	07
Q.2	(a) Describe the need of biasing the transistor.	03
	(b) Draw the symbol of NPN & PNP transistor, write its different operating regions and also explain why it is called as “Bipolar Transistor”.	04
	(c) Discuss Common Collector(CC) configuration of transistor and explain its input and output characteristics.	07
	OR	
	(c) Discuss Common Base(CB) configuration of transistor and explain its input and output characteristics.	07
Q.3	(a) Derive the relation between current gain α and β	03
	(b) Describe the factors affecting the Stability of Q point.	04
	(c) Explain the construction, working principle and application of phototransistor.	07
	OR	
Q.3	(a) Discuss about leakage current in transistor.	03
	(b) Write a short note on Thermal runaway.	04
	(c) Describe the construction, the symbol, V-I characteristics and application of Tunnel diode.	07
Q.4	(a) Discuss about transconductance curve of JFET.	03
	(b) Explain transistor as a switch.	04
	(c) Explain in detail different models used for AC analysis of BJT circuits.	07
	OR	
Q.4	(a) Write applications of JFET.	03
	(b) Explain the working of Emitter follower.	04

	(c)	Draw h parameter equivalent model for CE amplifier and derive the equation for input impedance, output impedance, Voltage gain and current gain for CE amplifier.	07
Q.5	(a)	Draw symbol, truth table and Boolean equation for EX-OR and EX-NOR gate.	03
	(b)	Compare different logic families.	04
	(c)	Explain the construction and principle of operation of Enhancement type P-channel MOSFET.	07
OR			
Q.5	(a)	Design AND, OR and NOT gate using NAND Gate.	03
	(b)	Explain Transistor Transistor Logic (TTL).	04
	(c)	Explain the construction, working and drain characteristics of N-Channel JFET.	07

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-I (NEW) EXAMINATION – WINTER 2023

Subject Code:3110016

Date:25-01-2024

Subject Name:Basic Electronics

Time:02:30 PM TO 05:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

MARKS

Q.1	(a) Draw symbol and truth table for AND, NOR, EX-OR logic gates.	03
	(b) Discuss forward and reverse bias operation of a P-N junction diode with depletion region.	04
	(c) Draw CB configuration and discuss its input and output characteristics with I_{CBO} , r_i , r_o , and current gain α .	07
Q.2	(a) Describe Negative clamper circuit with necessary waveforms	03
	(b) Describe RC filter with its limitations.	04
	(c) Draw circuit diagram of Center-taped full wave rectifier and explain its operation with necessary waveforms and derivation of V_{dc} .	07
	OR	
	(c) Describe diode approximations in detail.	07
Q.3	(a) Draw circuit for Voltage doubler and explain its operation.	03
	(b) Briefly explain the effect of coupling capacitor and bypass capacitor on small signal transistor amplifier.	04
	(c) Draw circuit for Emitter feedback bias and explain in detail with its advantages and disadvantages.	07
	OR	
Q.3	(a) State the difference between Avalanche breakdown and Zener breakdown.	03
	(b) Discuss Zener diode as voltage regulator.	04
	(c) Discuss load line, Q point, DC & AC load lines for BJT.	07
Q.4	(a) Derive relation between α & β for BJT.	03
	(b) Compare different BJT configurations.	04
	(c) Describe working principle and applications of PIN Photo diode and Solar cell.	07
	OR	
Q.4	(a) Briefly explain regions of operation for BJT.	03
	(b) Discuss seven segment displays with its types.	04
	(c) Draw CE configuration and discuss its input and output characteristics with I_{CEO} , r_i , r_o , and current gain β .	07

- Q.5** (a) Compare FET with BJT. **03**
(b) Explain FET as a switch. **04**
(c) State different logic families and compare them in terms of fan in, fan out, propagation delay, noise margin, power dissipation. **07**

OR

- Q.5** (a) Construct AND & OR gates with diodes. **03**
(b) Explain FET as an amplifier. **04**
(c) Explain Drain characteristics and Transfer characteristics of JFET in detail with all related terms as Transconductance g_m , drain resistance r_d , and amplification factor μ . **07**

Enrolment No./Seat No _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-I & II (NEW) EXAMINATION – SUMMER 2024

Subject Code:3110016

Date:06-07-2024

Subject Name:Basic Electronics

Time:02:30 PM TO 05:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

- Q.1** (a) Explain series positive clipper with diagram. 03
(b) Draw and explain V-I characteristic of P-N junction diode. 04
(c) Draw and Explain bridge rectifier. Explain advantage and disadvantage of bridge rectifier over full wave rectifier. 07
- Q.2** (a) Drive the relation between current gain α and β for CE configuration. 03
(b) Draw the symbol of NPN & PNP transistor. Also state the advantage of transistor. 04
(c) Draw and explain input and output characteristic of transistor in CE configuration. 07
- OR**
- (c) Compare CE, CB, and CC configuration with respect to different transistor characteristics. 07
- Q.3** (a) Explain V-I characteristics of tunnel diode. 03
(b) Explain Schottky diode in details. 04
(c) Comparison between P-N junction Diode and Zener Diode. 07
- OR**
- Q.3** (a) Advantage, disadvantage and application of LED. 03
(b) Compare PIN diode and Photo Diode. 04
(c) State the applications of Rectifier, and Comparison of Halfwave, Full-wave center- tap and Full-wave Bridge rectifier. 07
- Q.4** (a) List out the salient feature of emitter follower. 03
(b) Classification of Logic families in details. 04
(c) Explain application of Transistor as a switch. 07
- OR**
- Q.4** (a) Explain Negative Clamping circuit with diagram. 03
(b) Explain why NAND and NOR gate are called universal gate. 04
(c) Discuss MOSFET in details. 07
- Q.5** (a) Define the use of Coupling capacitor. 03
(b) Give Comparison of BJT and FET. 04
(c) Draw symbol and explain all logic gates in details. 07
- OR**
- Q.5** (a) Explain the properties and application of common base amplifier. 03
(b) State advantage, disadvantage and application of FET. 04
(c) Give comparison between different types of digital logic families. 07

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- SEMESTER-I & II EXAMINATION – WINTER 2024****Subject Code:3110016****Date:17-01-2025****Subject Name:Basic Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) Sketch the characteristics of ideal diode and approximate characteristics of practical diodes. Briefly explain it.	03
	(b) Draw two-diode full-wave rectifier circuit and explain its operation.	04
	(c) Explain positive and negative voltage clamper circuit with waveforms.	07
Q.2	(a) What are three modes of transistor operation, explain it.	03
	(b) What is you understand by transistor biasing and why it is required.	04
	(c) Compare CB, CE and CC configuration.	07
	OR	
	(c) Explain the operation of voltage divider bias circuit using an npn transistor and write its voltage and current equation.	07
Q.3	(a) What is photo-diode and how it works?	03
	(b) What is varactor diode, and explain how it works?	04
	(c) In CE amplifier has $h_{ie} = 2.1 \text{ K}\Omega$, $h_{fe} = 75$ and $h_{oe} = 1 \text{ }\mu\text{S}$, voltage divider resistance $R_1 = 68 \text{ k}\Omega$ and $R_2 = 56 \text{ k}\Omega$, $R_c = 3.9 \text{ k}\Omega$, $R_E = 4.7 \text{ k}\Omega$ and $R_L = 82 \text{ k}\Omega$. Calculate input impedance, output impedance and voltage gain.	07
	OR	
Q.3	(a) What is tunnel diode, and explain how it works?	03
	(b) Explain how Zener diode maintains constant voltage across load with circuit.	04
	(c) Draw single stage CE amplifier and analyze and explain how it works.	07
Q.4	(a) Define saturation current, pinch off voltage and transconductance in JFET.	03
	(b) Do comparison between BJT and FET and write it.	04
	(c) Analyze and explain CB amplifier and find its input impedance, output impedance and voltage gain	07
	OR	
Q.4	(a) Define performance parameter of JFET a.c. drain resistance, transconductance and amplification factor.	03
	(b) In n-channel JFET with $V_{GS(off)} = -6 \text{ V}$ and $I_{DSS} = 3 \text{ mA}$ Solve I_D value for $V_{GS} = -1, -3, \text{ and } -5 \text{ V}$.	04
	(c) Consider a CB amplifier utilizing a BJT biased at $I_c = 1 \text{ mA}$ with $R_c = 5 \text{ k}\Omega$, $R_L = 5 \text{ k}\Omega$. Determine R_{in} , A_{vo} , A_v , and R_o .	07
Q.5	(a) What is logic gates and state the rule used for OR and AND gate.	03
	(b) Why NAND and NOR gates are called universal gate and draw truth table of NAND gate.	04
	(c) Write and explain application of FET as amplifier and as a switch.	07

OR

- Q.5** (a) Draw the logic circuit for the Boolean expression $Y = ABC + \bar{D}$. **03**
(b) Explain Transistor Transistor Logic (TTL). **04**
(c) Using common source circuit have a $R_1 = 5.6 \text{ M}\Omega$, $R_2 = 1 \text{ M}\Omega$, $R_D = R_S = 2.7 \text{ K}\Omega$, $r_d = 100 \text{ K}\Omega$ and $Y_{fs} = 3000 \text{ }\mu\text{S}$ calculate input impedance, output impedance and voltage gain. **07**

GUJARAT TECHNOLOGICAL UNIVERSITY

BE- SEMESTER-I&II EXAMINATION – SUMMER 2025

Subject Code:3110016

Date:17-06-2025

Subject Name:Basic Electronics

Time:10:30 AM TO 01:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Draw and explain constructional details and symbols for BJT.	03
	(b) Draw and explain the V/I characteristics of a practical diode.	04
	(c) Draw Common Base configuration and discuss its input and output characteristics with I_{CBO} , r_i , r_o , and current α .	07
Q.2	(a) Define: clipper, Clamper, PIV of a Diode.	03
	(b) Compare different rectifier circuits.	04
	(c) Discuss diode approximations.	07
	OR	
	(c) Explain full wave center-tape rectifier in detail with waveforms and derivation of average output voltage.	07
Q.3	(a) Draw circuit diagram of positive clamper and explain the operation.	03
	(b) Draw and explain circuit of AND gate using diodes.	04
	(c) Explain thermal stability of BJT with stability factors S, S', S''.	07
	OR	
Q.3	(a) Draw Hybrid equivalent model of transistor for CB, CE, CC configurations.	03
	(b) Describe LED with its applications.	04
	(c) Discuss operation and applications of PIN Photo diode and Solar cell.	07
Q.4	(a) State the difference between Avalanche breakdown and Zener breakdown.	03
	(b) Discuss seven segment display with its types.	04
	(c) Explain biased positive and negative clipper circuits in detail.	07
	OR	
Q.4	(a) For a BJT, α_{dc} is 0.98 and base current is 50 μA , then find β_{dc} , I_C & I_E .	03
	(b) Compare CB, CE, CC configurations.	04
	(c) Draw Emitter follower circuit and discuss its input and output characteristics.	07
Q.5	(a) Compare BJT & FET.	03
	(b) Explain OR gate using diodes.	04
	(c) Describe MOSFET operation and draw the structures for D-MOSFET & E-MOSFET.	07
	OR	
Q.5	(a) Discuss FET as an amplifier.	03
	(b) Compare different logic families.	04
	(c) Explain Drain characteristics and Transfer characteristics of JFET in detail with all related terms as Transconductance, drain resistance and amplification factor.	07

GUJARAT TECHNOLOGICAL UNIVERSITY

BE- SEMESTER-I & II EXAMINATION – WINTER 2025

Subject Code:3110016

Date:19-01-2026

Subject Name:Basic Electronics

Time:02:30 PM TO 05:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	Marks
Q.1 (a) Draw the v_i characteristics for ideal diode and real diode.	03
(b) Explain the forward and reverse bias of PN junction.	04
(c) Discuss the operation of full bridge rectifier circuits with voltage and current waveforms.	07
Q.2 (a) Draw the circuits for clipping the voltage waveforms.	03
(b) Explain the characteristics of Zener diode.	04
(c) Write short note on bipolar junction transistor (BJT).	07
OR	
(c) Explain the operation of transistor as amplifier in Common Emitter(CE) configuration.	07
Q.3 (a) Write key factors to achieve faithful amplifications.	03
(b) Discuss the importances of operating points in transistor.	04
(c) Discuss the load line analysis of transistor.	07
OR	
Q.3 (a) What is a stability factor?	03
(b) Explain the voltage divider biasing.	04
(c) Discuss the construction and operation of Schottky diode.	07
Q.4 (a) What are the roles of coupling capacitor and bypass capacitor in amplifier circuits?	03
(b) Discuss the operation of common collector circuits analysis.	04
(c) Shows parametric comparisons between of CE, CB and CC.	07
OR	
Q.4 (a) Draw the circuits of seven segment LED display.	03
(b) What are the differences between FET and BJT?	04
(c) Write short note on MOSFET.	07
Q.5 (a) Prepare the truth table for three basic logic gates.	03
(b) Explain the working principle of a field effect transistor (FET).	04
(c) Discuss the resistor transistor logic (RTL)circuits for basic gates.	07
OR	
Q.5 (a) Draw the circuit diagram of OR gate with diodes.	03
(b) Show the implementation of OR gate logic with use of NAND gate.	04
(c) Discuss the applications of EX-OR and EX-NOR gate with truth tables.	07