

Parameter	CB Configuration	CE Configuration	CC Configuration
Circuit Diagram			
Input Characteristics			
Output Characteristics			
Common terminal between input and output	Base	Emitter	Collector
Input Current	I_E	I_B	I_B
Output Current	I_C	I_C	I_E
Current Gain	$\alpha_{dc} = \frac{I_C}{I_E}$	$\beta_{dc} = \frac{I_C}{I_B}$	$\gamma_{dc} = \frac{I_E}{I_B}$
Input Voltage	V_{EB}	V_{BE}	V_{BC}
Output Voltage	V_{CB}	V_{CE}	V_{EC}
Voltage Gain	Meduim	Medium	Less than 1
Input Resistance	Very Low (20 Ω)	Low (1K Ω)	High (500 K Ω)
Output Resistance	Very High (1 M Ω)	High (40 K Ω)	Low (50 K Ω)
Applications	As pre-amplifier	As Audio Amplifier	For Impedance Matching