

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER– VI (NEW) EXAMINATION – WINTER 2021****Subject Code:3160921****Date:04/12/2021****Subject Name:HVDC Transmission Systems****Time:10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Compare AC and DC Transmission in view of economy and reliability.	03
	(b) Describe selective harmonic elimination technique.	04
	(c) Describe the schematic diagram of a HVDC link, mentioning all the key elements.	07
Q.2	(a) Write types of HVDC systems.	03
	(b) Explain six pulse converter with neat diagram.	04
	(c) Explain effects of firing angle delay in line commutated converters.	07
	OR	
	(c) Explain twelve pulse converters.	07
Q.3	(a) Classify PWM techniques.	03
	(b) Explain rotating reference frame theory.	04
	(c) Explain real and reactive power control using VSC.	07
	OR	
Q.3	(a) Explain starting and stopping of HVDC link.	03
	(b) Explain principles of DC Link Control in a VSC based HVDC system.	04
	(c) Write short note on high level controllers.	07
Q.4	(a) Explain corona effect.	03
	(b) Enlist different types of insulators. Explain all in short.	04
	(c) Draw Phase locked loop diagram. Explain its working in detail.	07
	OR	
Q.4	(a) Enlist reactive power sources in HVDC system.	03
	(b) Explain basic concept of power system angular control.	04
	(c) Explain basic principles of synchronous and asynchronous links.	07
Q.5	(a) Write types of Multi-terminal HVDC System.	03
	(b) Explain Mono-polar Operation of HVDC link.	04
	(c) Write short note on DC circuit breakers.	07
	OR	
Q.5	(a) What is modular multilevel converter?	03
	(b) Explain Parallel Operation of HVDC.	04
	(c) Write notes on voltage stability problems in HVAC/DC systems.	07
